




Mux3to1 : a 3 to 1 multiplexer, choose the result that is going to write back, control by FURslt, control signal from ALU\_Ctrl

Shifter: shift the input by a given number and output the result, used for sll / slr instr.


Sign\_Extend: extend the input, used for extending the constant of immediate instr.

### 3. Finished Part:


test data 1:

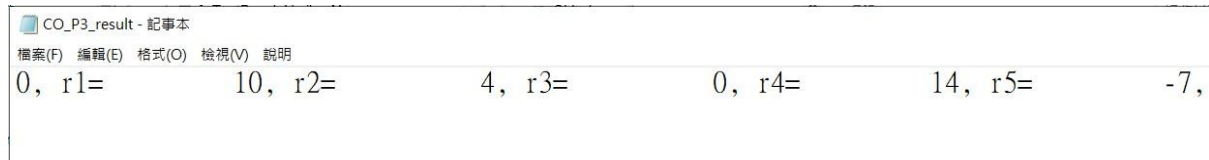

test data 2:

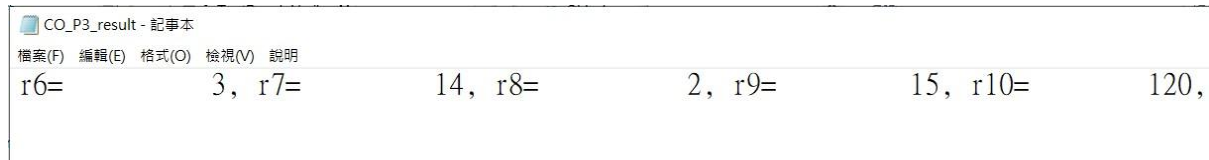

test data 3:

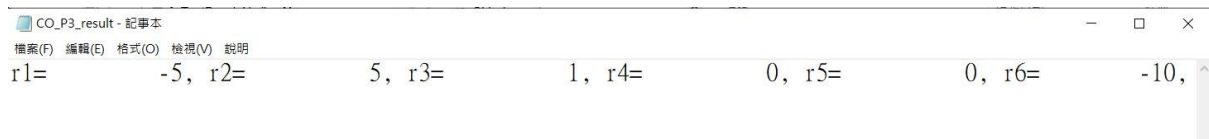

### 4. Problems you met and solutions:

- (1) put the txt. into the project  
solution: I try to put them in design source and simulation source, and find out that I should put them in simulation source.
- (2) using ?: as a wrong way  
I use nested structure, and it shows errors. Then I think for a long time and find out that I miss the value when none of the conditions fit.
- (3) connect wrong wire  
I draw a diagram on the paper and check through every block's input and output, then can easily find out the wrong wire.

### 5. Summary

- (1) I learned how to implement a simple cycle cpu and connect wires. Also use assign in a proper way.
- (2) more debugging ways, like debug block by block, and I display the wire data to check if the answer is correct or not.